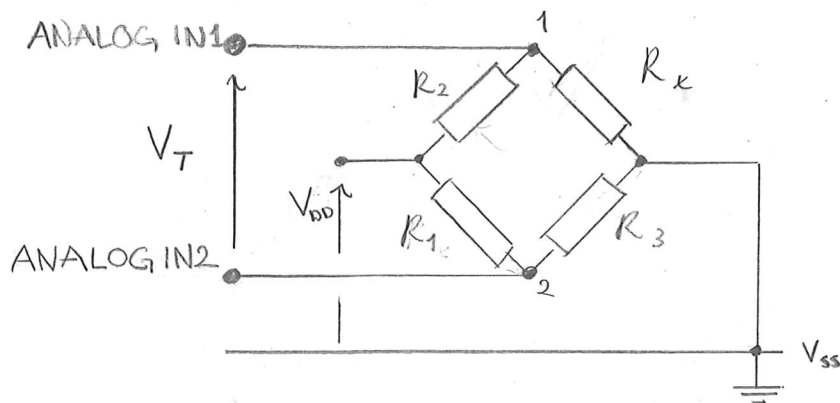


Analog Temp. Circuit



$$V_{DD} - V_{SS} = V \quad (V_{SS} = 0V)$$

$$V_T = V_1 - V_2 = \frac{R_x}{R_2 + R_x} V - \frac{R_3}{R_1 + R_3} V$$

$$\left[\frac{V_T}{V} + \frac{R_3}{R_1 + R_3} \right] (R_2 + R_x) = R_x$$

$$\left[\frac{V_T}{V} + \frac{R_3}{R_1 + R_3} \right] R_2 = R_x \left[1 - \frac{V_T}{V} - \frac{R_3}{R_1 + R_3} \right]$$

$$\Rightarrow \underline{R_x} = \frac{R_2 \left(\frac{V_T}{V} + \frac{R_3}{R_1 + R_3} \right)}{1 - \frac{V_T}{V} - \frac{R_3}{R_1 + R_3}} = \frac{R_2}{\frac{V(R_1 + R_3)}{V_T(R_1 + R_3) + VR_3} - 1}$$

$$\left(\frac{V_T}{V} + \frac{R_3}{R_1 + R_3} \right)^{-1} = \frac{V(R_1 + R_3)}{V_T(R_1 + R_3) + VR_3}$$

$$R_x = \frac{R_2}{\frac{R_1/R_3 + 1}{V_T/V(R_1/R_3 + 1) + 1} - 1}$$

Pt100, Pt500 and Pt1000 resistors belong to a standardised series. The document defining this standard is the European "EN 60 751".

Pt100 - $100 \Omega @ 0^\circ\text{C}$

Pt500 - $500 \Omega @ 0^\circ\text{C}$

Pt1000 - $1000 \Omega @ 0^\circ\text{C}$

The relation of temperature-to-resistance is polynomial:

$$R(T) = \begin{cases} R_0(1 + AT + BT^2 + C[T - 100^\circ\text{C}]T^3), & T \in (-200^\circ\text{C}, 0^\circ\text{C}) \\ R_0(1 + AT + BT^2), & T \in (0^\circ\text{C}, 850^\circ\text{C}) \end{cases}$$

where

$$A = 3.90802 \times 10^{-3} \text{ } ^\circ\text{C}^{-1},$$

$$B = -5.775 \times 10^{-7} \text{ } ^\circ\text{C}^{-2},$$

$$C = -4.2735 \times 10^{-12} \text{ } ^\circ\text{C}^{-4},$$

T is temperature in $^\circ\text{C}$,

R_0 is resistance @ 0°C in Ω

Resistance-to-temperature:

Above 0°C :

$$T(R) = \frac{-R_0 A + \sqrt{(R_0 A)^2 - 4B(R_0 - R)}}{2 R_0 B}$$

Iteration for below 0°C :

$$T_{i+1} = T_i - \frac{R(T_i) - R}{R'(T_i)} = T_i - \frac{R_0(1 + AT_i + BT_i^2 + C[T_i - 100^\circ\text{C}]T_i^3) - R}{R_0(A + 2BT_i + C[3T_i^2(T_i - 100^\circ\text{C}) + T_i^3])}$$

To set appropriate bridge resistor values, we need to set a range to be measured. Setting $\pm 50^\circ\text{C}$, we get the range $(R(-50^\circ\text{C}), R(50^\circ\text{C}))$.

$$\begin{aligned} R(-50^\circ\text{C}) &= 80.3 \, \Omega & \text{Pt100} \\ &401.5 \, \Omega & \text{Pt500} \\ &803.1 \, \Omega & \text{Pt1000} \end{aligned}$$

$$\begin{aligned} R(50^\circ\text{C}) &= 119.4 \, \Omega & \text{Pt100} \\ &597.0 \, \Omega & \text{Pt500} \\ &1194.0 \, \Omega & \text{Pt1000} \end{aligned}$$

Looking back at the equation for V_T (measured voltage):

$$V_T = V \left(\frac{R_x}{R_1 + R_x} - \frac{R_3}{R_2 + R_3} \right)$$

Setting $R_1 = R_2$ and $R_3 = R_x(T)|_{T=T_{\min}}$, we get $V_T = 0\text{V}$ at T_{\min} , the smallest measurable temperature.

Now to set $R = R_1 = R_2$. We want maximum V_T available. Looking at the above equation and taking the derivative w.r.t. R :

$$\text{Res } \frac{dV_T/V}{dR} = - \frac{R_x}{(R+R_x)^2} + \frac{R_3}{(R+R_3)^2} = 0$$

$$\Rightarrow R_x (R^2 + 2RR_3 + R_3^2) = R_3 (R^2 + 2RR_x + R_x^2)$$

$$\Rightarrow R^2 (R_x - R_3) + R_x R_3^2 - R_3 R_x^2 = 0$$

$$\Rightarrow R = \left[\frac{R_3 R_x^2 - R_x R_3^2}{R_x - R_3} \right]^{1/2}$$

We now have three cases (PT100, PT500, PT1000) for a given temperature range. The three cases are compared for total current consumption and output voltage range V_T .

The range, given that $V_T = 0V \Big|_{T_{min}}$, is $V_T \Big|_{T_{max}}$.

After extensive MATLAB analysis, the following is concluded:

1. The thermistors have current limits to

be met;	Limit (mA)	Recommended (mA)
from datasheet →	PT100	7
	PT500	3
	PT1000	1

2. In order to meet these ratings, current limiting resistors placed in series with R_4 and $R_x(T)$ are needed.

3. Additionally, $R = R_1 = R_2$ need to be increased by about a factor 4 to reach the current ratings, relative $R \Big|_{V_{Tmax}}$.

4. V_{Tmax} resulting in the $10^2 \sim 10^3$ mV range necessitates amplification. The low supply voltage and output resistance can be compensated by a low-power, rail-to-rail instrumentation amplifier.

So, the result is:

PT1000 JUMO 00409849

MAX4460 Instrumentation Amplifier *

$$R = R_1 = R_2 = (8.2k\Omega \parallel 270k\Omega) \approx 7955.75\Omega$$

$$R_3 = 1.8k\Omega$$

Desired gain $\sim 29.4 \Rightarrow R_{FB2}, R_{FB1}$ setting the gain

$$\rightarrow R_{FB2} = 330k\Omega, R_{FB1} = 12k\Omega, G = 28.5$$

or

$$\rightarrow R_{FB2} = 100k\Omega, R_{FB1} = 2.7k\Omega + 820\Omega, G = 29.41$$

$$R_{FB2} = 330k\Omega, R_{FB1} = (12k\Omega \parallel 390k\Omega), G = 29.35$$

0.1 μ F in-amp decoupler

$$R_{limiter} = 1k\Omega$$

